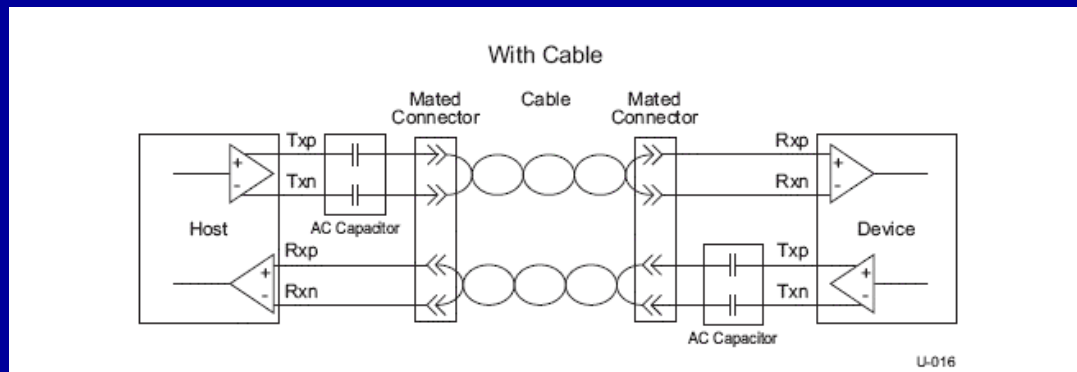


USB3.0 Channel Simulation Schematic

USB channel schematics with cable




Test circuit

Input Signal Source

Cable

CTLE (*Continuous Time Linear Equalizer*)

 

USB3.0 Channel Simulation

Components

◆ Input Signal: PRBS

```
Voutp inp 0 PWL(  
+ 0.00000000e+000 -0.800000  
+ 3.00000000e-011 0.800000  
+ 2.00000000e-010 0.800000  
+ 2.30000000e-010 -0.800000  
...
```


◆ Cable: 4-port transmission line Macro-model

```
xcable inp inn n3 n4 skewcable3m_passive  
.subckt skewcable3m_passive a_1 a_2 a_3 a_4  
VI_1 a_1 NI_1 0  
RI_1 NI_1 ref 5.0000000000000000e+001  
GC_1_1 ref NI_1 NS_1 0 -1.6802855942555286e+001  
...  
.ends
```

USB3.0 Channel Simulation Components

◆ CTLE: Continuous Time Linear Equalizer

 E1 0 outn Laplace 0 n4 2.5659E+20 6.286E+10 /
3.845244E+20 4.3646E+10 1.0




It act as High-Pass filter at 750MHz, then act gain Amplifier at 750MHz to 7.5GHz, then act as Low-Pass filter at over 7.5GHz to compensate Cable Loss


USB3.0 Channel Simulation

MSIM-PCB Simulation Results

Input Signal

 


Output Signal

 

USB3.0 Channel Simulation

Eye-Diagram

Eye Diagram

 

Eye Width (UI):
400 p sec
Trigger Period:
0.5 UI

**Verification
Standards:**

- ...
- Minimum eye height
- Minimum eye width
- ...

MSIM[®] Certifications

- ◆ JEITA (Japan Electric and Information Technology Industries Association) has qualified MSIM-PCB for simulating IBIS models in PCB designs. Those results can be downloaded from JEITA web:

<https://ec.jeita.or.jp/ibis/>

- ◆ MSIM certified by TSMC's Spice Tool Qualification Program

<http://www.legenddesign.com/BW/021009.shtml>